 



Name : Abdul Ghani Khan.  
 Section : BS-CS 2A  
 Roll.No: 22P-9037  
 Instructor: SIR SULEMAN MIR  
 DLD ASSIGNMENT # 02

### Question A :-

1. Write the output expression for each circuit in



$$X = A' + A'B + AC \text{ / Ans.}$$

 


$$* A'B + A'CD + DBD'$$


Now lets pass them from the not gate.

$$X = AB' + AC'D' + D'B'D \text{ / Ans.}$$

 
2. Write the output expression for each circuit as it appears in.




$$X = AB \cdot B$$

 


$$X = AB + B$$

 


$$X = A' + B$$

 

$$X = (A+B) + AB$$

 

$$X = AB \cdot B \cdot C$$

 

$$X = (A+B) \cdot (B'+C)$$



will as

### Question C:

\* Question B at end.

For each set of binary numbers, determine the output states for the comparator of Figure 6-21.

$$(a) \quad A_3 A_2 A_1 A_0 = 1010 \\ B_3 B_2 B_1 B_0 = 1101$$

Let start by comparing each bit from MSB

$$A_3 = 1, \quad B_3 = 1 \quad A_3 = B_3.$$

Let move on to the next as we can't decide from this one,

$$B_2 = 1, \quad A_2 = 0 \quad A_2 < B_2.$$

There's no point of comparing the rest but let's do it as the comparator will do and then mark it in our case.

$$A_1 = 1, \quad B_1 = 0 \quad A_1 > B_1 \text{ (D.C.)}$$

$$A_0 = 0, \quad B_0 = 1 \quad A_0 < B_0 \text{ (D.C.)}$$

Output :-

Hence the output states are,

$A < B = 1$  (High) and the rest are low which are,

$$A > B = 0 \text{ and } A = B = 0$$

$$(b) \quad A_3 A_2 A_1 A_0 = 1101 \\ B_3 B_2 B_1 B_0 = 1101$$

comparing bit by bit.

$$A_3 = B_3 = 1.$$

$$B_2 = A_2 = 1.$$

$$A_1 = B_1 = 1.$$

$$A_0 = B_0 = 1.$$

(+C)

$$A = B.$$

Output :-

Hence,  $A = B = 1$  (High) and the others are Low that are,

$$A < B = 0, \quad A > B = 0$$

$$(C) \quad A_3 A_2 A_1 A_0 = 1001$$

$$B_3 B_2 B_1 B_0 = 1000$$

Comparing bit by bit,

$$A_3 = 1, \quad B_3 = 1 \quad A_3 = B_3.$$

$$A_2 = 0, \quad B_2 = 0 \quad A_2 = B_2.$$

$$A_1 = 0, \quad B_1 = 0 \quad A_1 = B_1.$$

$$A_0 = 1, \quad B_0 = 0 \quad A_0 > B_0.$$

So  $A > B$ .

Output :-


Hence  $A > B = 1$  (High) and the others are Low that are,

$$A = B = 0, \quad A < B = 0$$

Question D :-


Show that the decoding logic for each of the following codes if an active HIGH (1) output is required.

(a) 1101

 





(b) 1000.

 


(g) 000101.

 


(c) 11011

 


(h) 1110110

 


(d) 11100

 

(e) 101010

 


(f) 111110

 
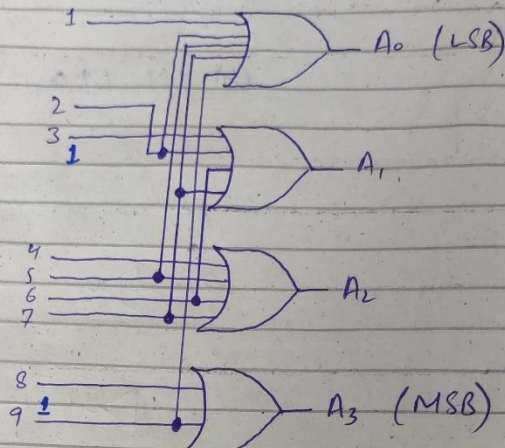
### Question E:-

Basic logic diagram of a decimal to BCD encoder. A 0-input is not needed because the BCD outputs are all LOW when there are no HIGH inputs.



- For the decimal-to-BCD encoder logic of the above figure assume that the 9 input and the 3 input are both HIGH. What is the output code? Is it a valid BCD (8421) code?

#### Output :-

$$A_3 = 1, A_2 = 0, A_1 = 1, A_0 = 1$$

$A_3 A_2 A_1 A_0 = 1011$  and its an invalid BCD.

#### Reason :-


It's an invalid BCD, as in BCD decimal digit is represented by 4-bit binary code which ranges from (0000 - 1001) or (0-9) but it is 1011 or 11 which is invalid.


 
### Question F:

For the multiplexer in the Below Figure, determine the output for the following input states:

$$D_0 = 1, D_1 = 0, D_2 = 0, D_3 = 1, S_0 = 0, S_1 = 1$$



As we know the multiplexer output expression:

$$\text{Output} : D_0 \overline{S_1} \overline{S_0} + D_1 \overline{S_1} S_0 + D_2 S_1 \overline{S_0} + D_3 S_1 S_0$$

and also putting the values.

$$\text{Output} : 1 \overline{1} \overline{0} + 0 \overline{1} \overline{0} + 0 \overline{1} \overline{0} + 1 \overline{1} \overline{0}$$

$$\text{Output} : 1 \overline{0} \overline{1} + 0 \overline{0} \overline{0} + 0 \overline{0} \overline{1} + 1 \overline{0} \overline{1}$$

$$\text{Output} : 0 + 0 + 0 + 0$$


$$\boxed{\text{Output} = 0}$$

### Question G:

Can a demultiplexer be used as a multiplexer?

If we talk only about using a demux alone then we cannot perform such action because both circuit have own operation,

 But technically it is possible, we can use a demultiplexer as a multiplexer by using a Demux circuit & a Mux is to perform the action that is,



### Question B:

1. What is a Full-Adder, also draw the complete logic circuit for Full Adder.

For the full adder of your logic diagram, determine the outputs for each of the following inputs.

Full Adder :-


A full Adder is a digital logic circuit that adds three binary digits or even more when used multiple, also gives a carry bit as output.

It is used to perform addition of two binary number of any length. The three or more input bits



are usually referred to as  $A$ ,  $B$  and  $C_{in}$ , where  $A$  and  $B$  are the bits to be added and  $C_{in}$  is the carry-in bit from the previous stage.

• Logic Circuit :-

 

(a)  $A = 0, B = 1, C_{in} = 0$

$Sum = 1, Carryout = 0.$

(b)  $A = 1, B = 0, C_{in} = 1.$

$Sum = 0, Carryout = 1.$

(c)  $A = 0, B = 0, C_{in} = 0$

$Sum = 0, Carryout = 0.$


2. What is half adder?

What are the half-adder inputs that will produce the following outputs,

• Half Adder:-

A digital circuit that performs addition operation on a 2 input binary values gives 2 outputs that is sum and carry out.

• Logic Circuit :-

 

(a)  $\Sigma = 0$  ,  $\text{Carry} = 0$

The inputs that will produce this are,

$A = 0$  and  $B = 0$ .

(b)  $\Sigma = 1$  ,  $\text{Carry} = 0$

The inputs that will produce this are,

$A = 1$  and  $B = 0$  or  $B = 1$  and  $A = 0$ .

(c)  $\Sigma = 0$  ,  $\text{Carry} = 1$ .

The inputs that will produce this output are,

$A = 1$  and  $B = 1$ .

THE END.