
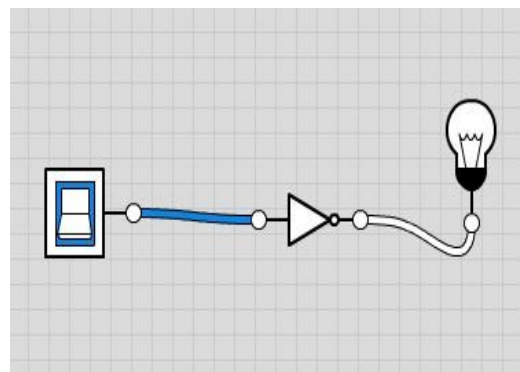


Name : ABDUL GHANI KHAN

Section: BCS-2A2




Roll-No: 22P-9037

Logic NOT Gate:

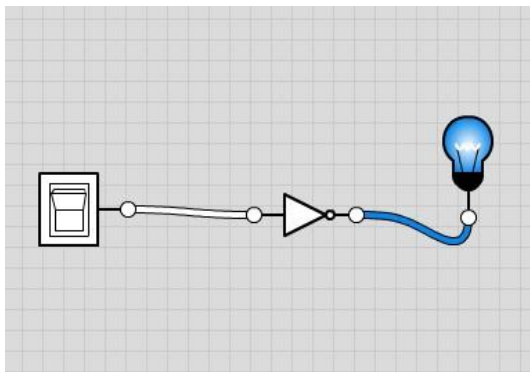


Input	output
0	1
1	0

Logic AND Gate:

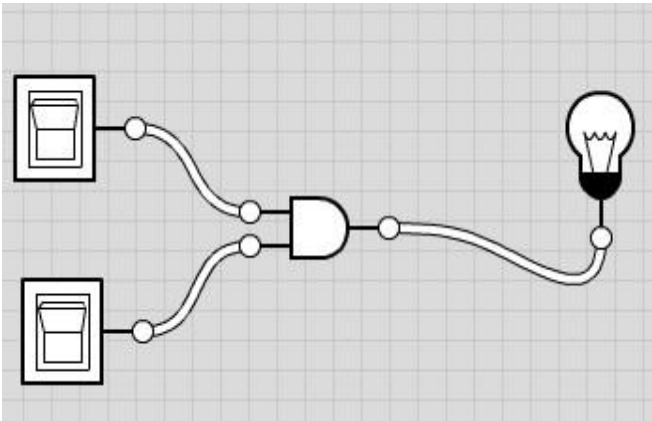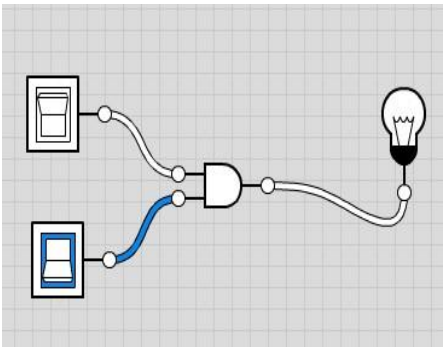
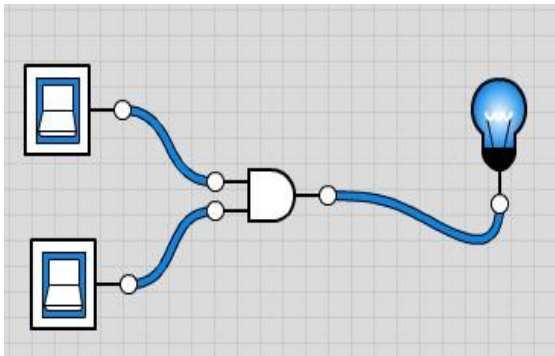


input(A)	input(B)	output(X)
0	1	0
0	0	0
1	0	0
1	1	1


Logic NAND Gate:

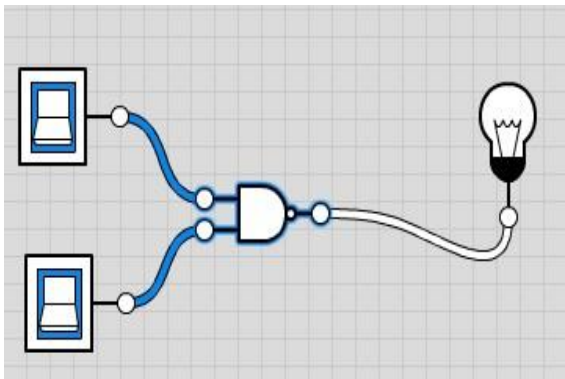



Input(A)	input(B)	output(X)
0	0	1
0	1	1
1	0	1
1	1	0

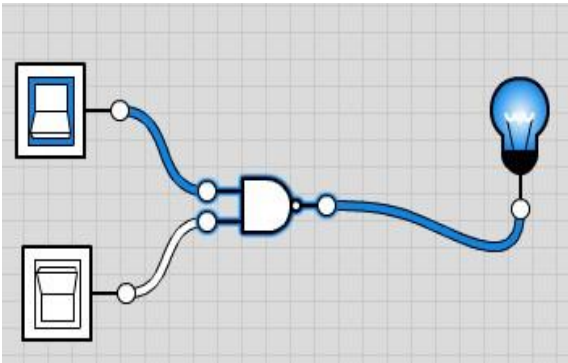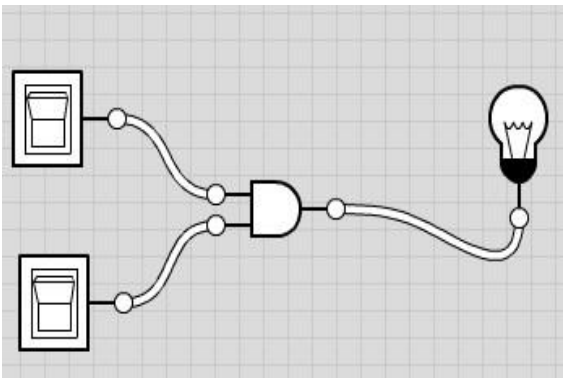

Logic OR Gate:

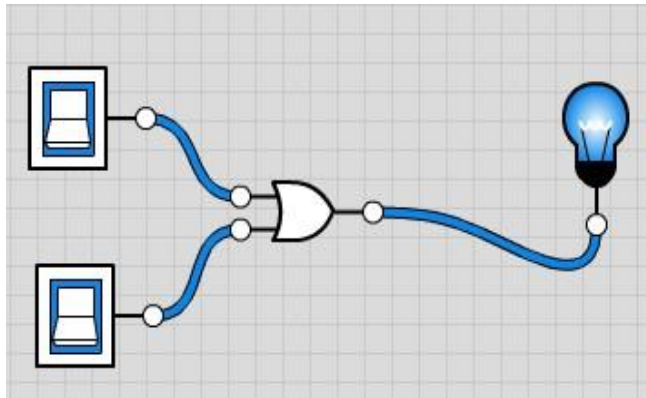


Input(A)	Input(B)	Output
0	1	1
1	0	1
1	1	1
0	0	0

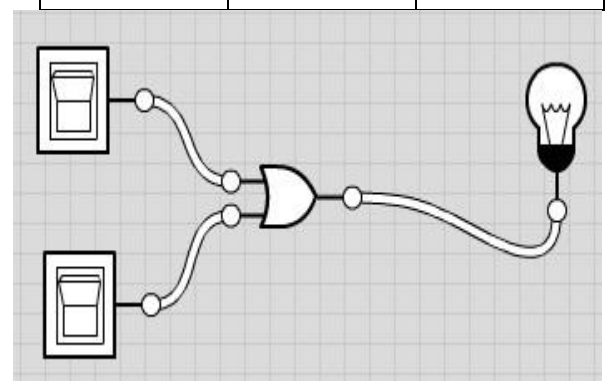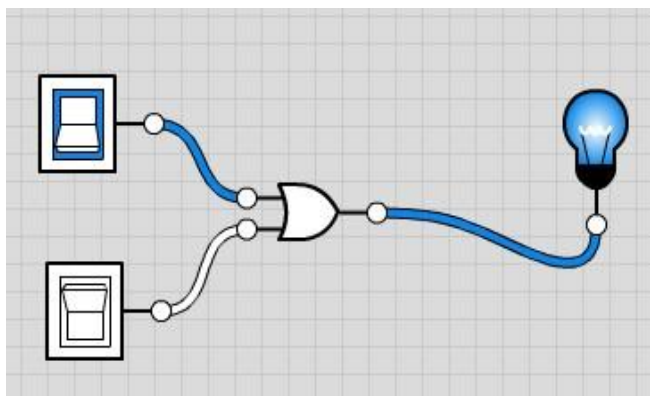



Logic NOR Gate:

The Logic NOR Gate is a combination of the digital logic OR gate and an inverter or NOT gate connected together.

Input(A)	Input(B)	Output
0	0	1
0	1	0
1	0	0
1	1	0



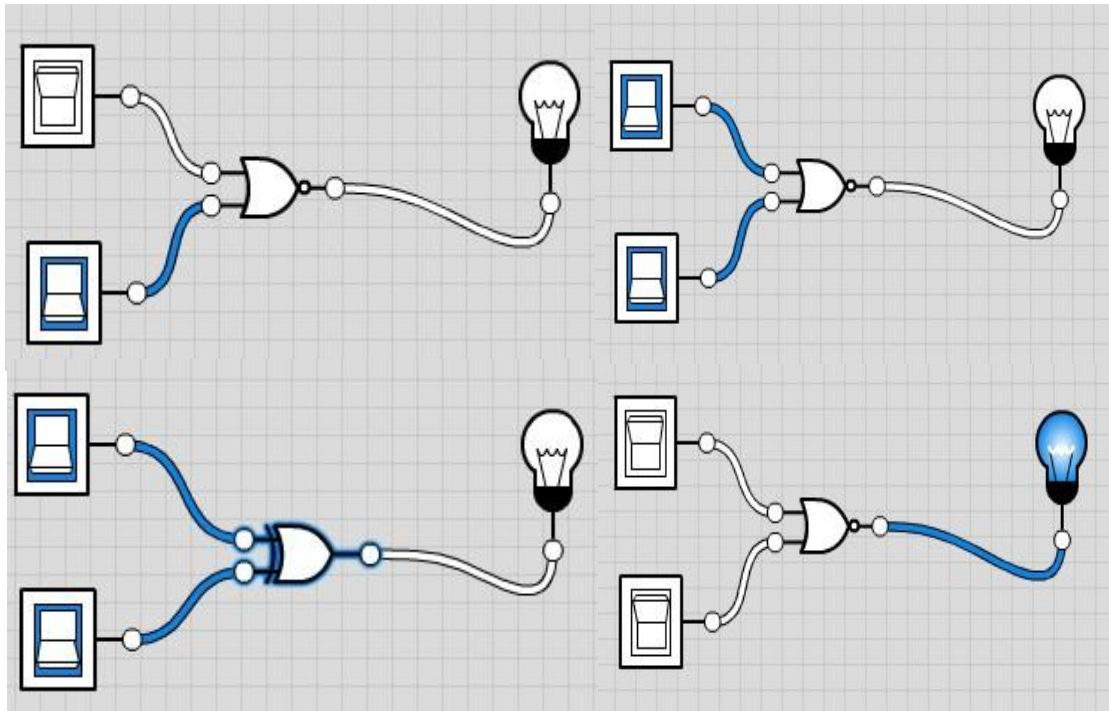


Exclusive-OR Gate:

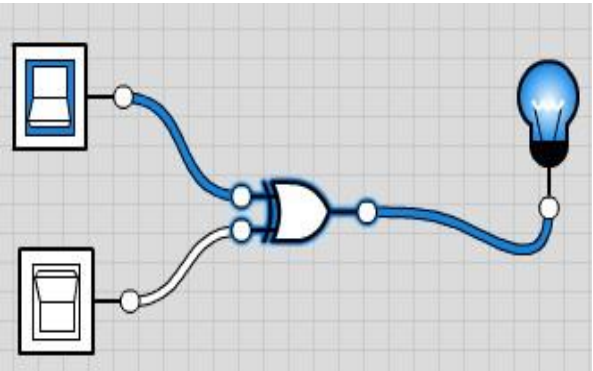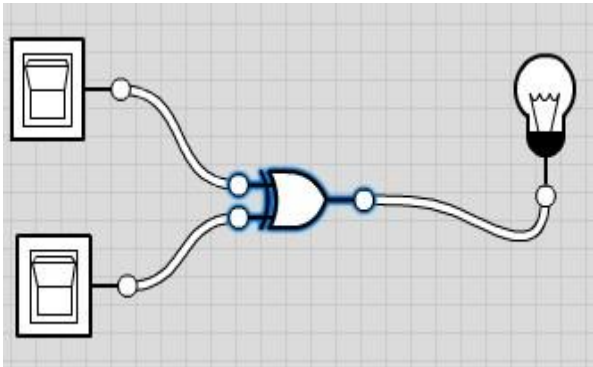

Input(A)	Input(B)	Output
0	0	0
0	1	1
1	0	1
1	1	0

Exclusive-NOR Gate:

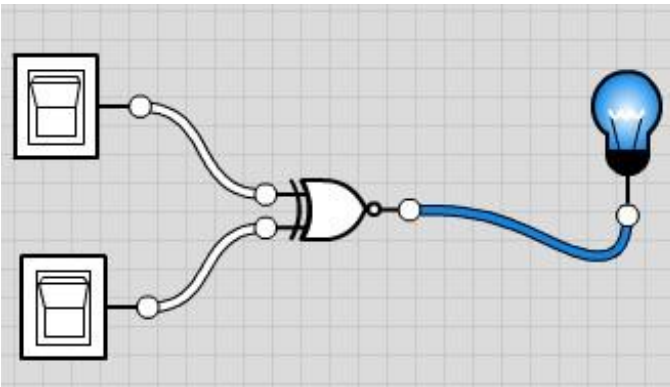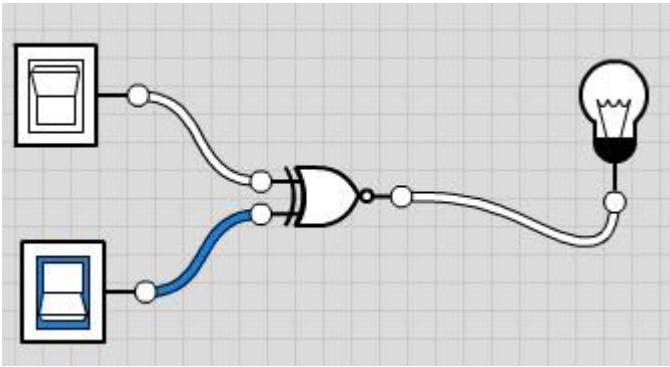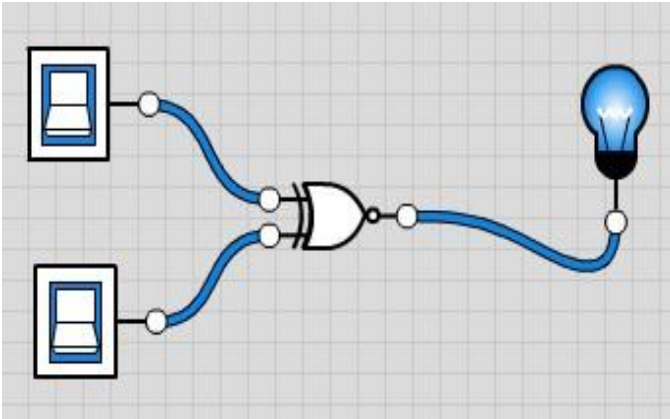

Input(A)	Input(B)	Output
0	0	1
1	0	0
0	1	0
1	1	1